# UL40-S2 with Auto-Bias and modified Ig2 compensation

This document describes implementation of the Tentlabs/Vanderveen Auto-Bias unit in the UL40-S2 valve amplifier modified with  $I_{g2}$  compensation to achieve lower  $2^{nd}$  harmonic distortion, after 'Vanderveen Trans Tube Amplifiers, figure 7-4, page  $58'^1$ .

#### Introduction:

The Tentlabs/Vanderveen Auto-Bias unit is aimed at keeping  $I_{cathode}$  constant and identical for both output tubes. The toroidal output transformers however require that  $I_a$  is identical for both tubes to achieve lowest distortion. Since  $I_{g2}$  is part of  $I_{cathode}$  (for pentode, UL and Super-triode configurations), and can vary from one valve to the next,  $I_a = (I_{cathode} - I_{g2})$  could vary too.

Menno van der Veen describes a neat solution to correct for this current difference in his book Trans Tube Amplifiers for his Trans-30 amplifier. Why not modify the UL40-S2 the same way? Below is shown what is needed, and further on the results are presented.

### **Schematics:**

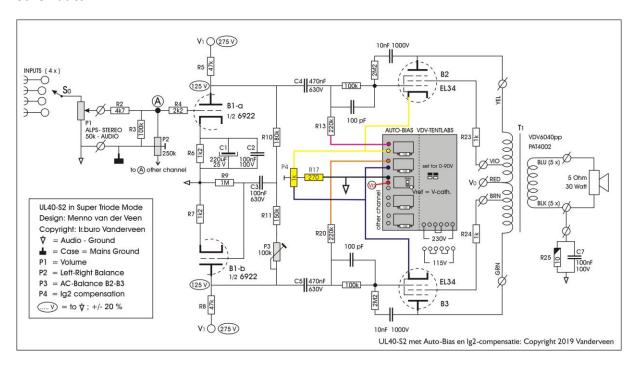


Fig. 1: UL40-S2 Auto-Bias circuit with  $I_{g2}$  compensation

The following components are added:

- P4 = 1k trim pot
- R17 = 270R

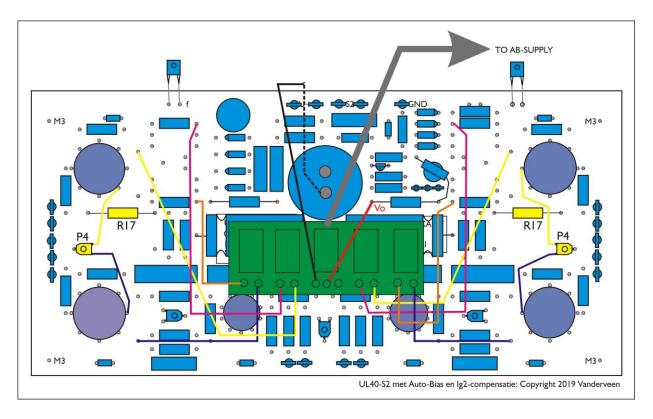


Fig. 2: PCB layout

- The runner of P4 is mounted to the original connection of C6 (positive side). Wire the two legs of P4 to the corresponding cathodes of B2 and B3.
- R17 (originally the cathode resistor) is enlarged to 270  $\Omega$ .

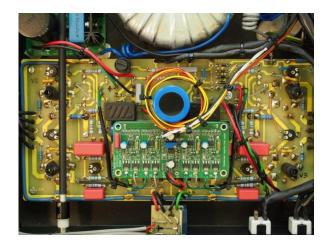


Fig. 3: UL40-S2 with Auto-Bias unit

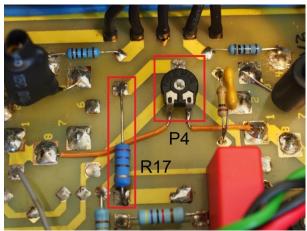


Fig. 4: Detail of P4 and R17 placement

# **Results:**

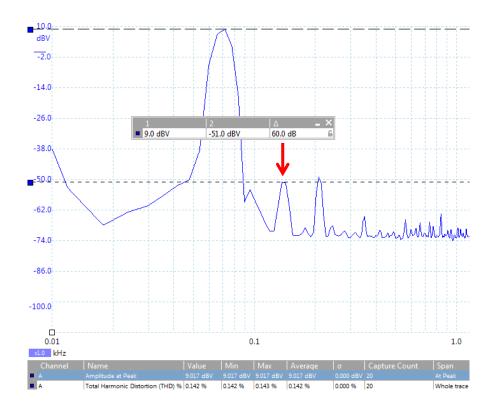


Fig. 5: AB test with 70 Hz test signal +9 dBV (= 1 W in 8  $\Omega$ ) With P4 in its mid position, no adjustment is made for differences in I<sub>g2</sub>.  $2^{nd} \text{ harmonic} = -60 \text{ dB} = 0,1 \%$ 

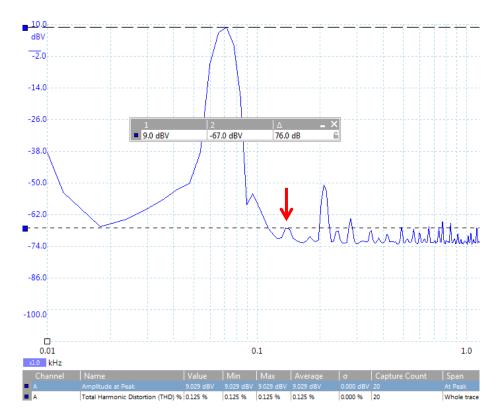


Fig. 6: AB test with 70 Hz signal +9 dBV (= 1 W in 8  $\Omega$ ) P4 is adjusted to minimize the 2<sup>nd</sup> harmonic component. 2<sup>nd</sup> harmonic now is -76 dB = 0,016 %

# **Conclusion:**

The above shows the benefit of implementing an extra trim pot to optimize the  $I_{g2}$  balance with the use of the Tentlabs/Vanderveen Auto-Bias unit. As a result, the  $2^{nd}$  harmonic distortion at 70Hz was reduced from 0,1 % to 0,016 %.

Zuidwolde, May 2019 Arjen van den Hoek arjenvandenhoek@hotmail.com

### Literature:

1: Menno van der Veen: "Vanderveen Trans Tube Amplifiers"; ISBN 978 1907 9203 49; <u>www.elektor.com</u> available as e-book



Fig. 7: UL40-S2 Valve Amplifier